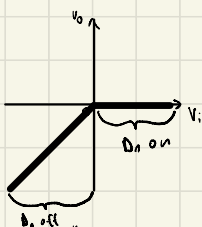


Exercise 4.


Robert Jakube

g.


a)




b)

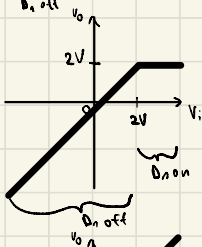


c)

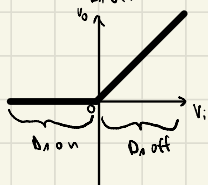


d)

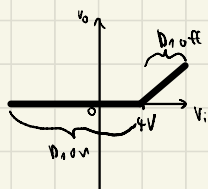


e)

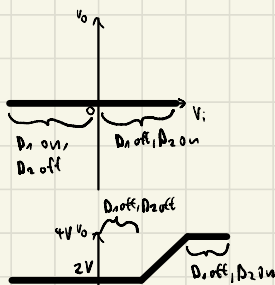

f)

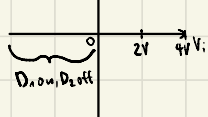

g)

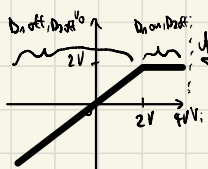


D_1 on, if: $V_{in} > 2V$

D_2 on, if: $V_{in} > 4V \Rightarrow$ If $V_{in} > 4V$: $V_{in} = 2V + 4V$

This circuit is not functional

10.

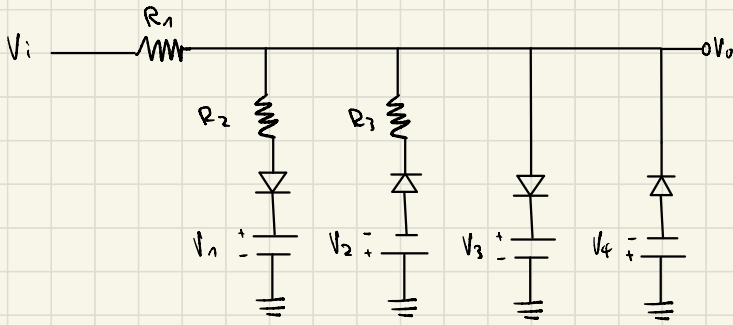

$$V_1 = V_2 = 2V; V_3 = V_4 = 4V$$

$$\frac{R_2}{R_2 + R_1} = \frac{R_3}{R_3 + R_1} = \frac{1}{2} \rightarrow \text{For example: } R_1 = R_2 = R_3 = 1k\Omega$$